

---

# ECE745: PROJECT1: LC3 INSTRUCTION SET ARCHITECTUE

---

---

## Disclaimer

*All the contents in this presentation have been repeated (in large part) with permission from ECE406 Notes for Spring 2007, ECE NCSU (Dr Rhett Davis, Dr Xun Liu).*

---

# LC-3 Instruction Set Architecture

---

- 16-bit wide memory
    - Each word is 2-bytes wide
    - The memory space has  $2^{16}$  words
  - 8 general purpose registers (Register File)
    - Can be a source/destination
  - Data type: 2s complement integers
  - 15 instructions
    - a) ALU      b) Control      c) Memory
  - Status register:
    - 3-bit **NZP**: **N**egative **Z**ero **P**ositive  
Captures the nature of latest entry in register file
  - PC: Program Counter: Points to instruction memory *i.e.* instruction = InstrMem[PC]
-

# LC-3 Instruction Set Architecture

---

- Opcode: unique for each instruction
    - $IR[15:12]$ ;  $IR = \text{instr. register} = \text{InstrMem}[PC]$
  - Addressing mode
    - Immediate (with sign extension) ( $[DR] \leftarrow [SR1] \ \& \ \text{signextend}(\text{Imm})$ )
    - Register (SR1 SR2) ( $[DR] \leftarrow [SR1] + [SR2]$ )
    - Memory:
      - PC relative  $\text{Mem}[PC + \text{signextend}(\text{Offset})]$
      - Indirect  $\text{Mem}[\text{Mem}[PC + \text{signextend}(\text{Offset})]]$
      - Base register +offset  
 $\text{Mem}[\text{BaseR} + \text{signextend}(\text{Offset})]$
-

# ALU Operation Instructions

---

	15	12	11	9	8	6	5	4	3	2	0
ADD	0 0 0 1				DR	SR1		0	0 0		SR2
	0 0 0 1				DR	SR1		1	imm5		
AND	0 1 0 1				DR	SR1		0	0 0		SR2
	0 1 0 1				DR	SR1		1	imm5		
NOT	1 0 0 1				DR	SR1			111111		

# ALU Operation Instructions

- Also called “Operate” Instructions
- AND       $IR[15:12] = 0101$ 
  - AND DR, SR1, SR2 ; **IR[5]=0**; ( $[DR] \leftarrow [SR1] \& [SR2]$ )
  - AND DR, SR1, Imm ; **IR[5]=1**; ( $[DR] \leftarrow [SR1] \& Imm$ )
- ADD       $IR[15:12] = 0001$ 
  - ADD DR, SR1, SR2 ; **IR[5]=0**; ( $[DR] \leftarrow [SR1] + [SR2]$ )
  - ADD DR, SR1, Imm ; **IR[5]=1**; ( $[DR] \leftarrow [SR1] + Imm$ )
- NOT       $IR[15:12] = 1001$ 
  - NOT DR, SR1      ( $[DR] \leftarrow \sim[SR1]$ )

Note: Imm is going to be sign extended to 16 bits for all computation.

# Memory Operations

---

	15	12	11	9	8	6	5	4	3	2	0
LD	0	0	1	0	DR	PCOffset9					
LDR	0	1	1	0	DR	BaseR		Offset6			
LDI	1	0	1	0	DR	PCOffset9					
LEA	1	1	1	0	DR	PCOffset9					
ST	0	0	1	1	SR	PCOffset9					
STR	0	1	1	1	SR	BaseR		Offset6			
STI	1	0	1	1	SR	PCOffset9					

# Memory Operations

---

- Load Effective Address
    - LEA DR, Offset    ( $[DR] \leftarrow PC+1+Offset$ )  
Offset = sxt(PCOffset9)
  - Load/Store (PC relative addressing mode)
    - LD DR, Offset    ( $[DR] \leftarrow \mathbf{MEM}[PC+1+Offset]$ )
    - ST SR, Offset    ( $\mathbf{MEM}[PC+1+Offset] \leftarrow [SR]$ )  
Offset = sxt(PCOffset9)
  - Load/Store Register  
(Base+Offset addressing mode)
    - LDR DR, BaseR, Offset  
( $[DR] \leftarrow \mathbf{MEM}[BaseR+Offset]$ )
    - STR SR, BaseR, Offset  
( $\mathbf{MEM}[BaseR+Offset] \leftarrow [SR]$ )  
Offset = sxt(PCOffset6)
-



# Memory Operations

---

- Load/Store Indirect (indirect addressing mode)

- LDI DR, Offset

- $(DR \leftarrow \mathbf{MEM}[\mathbf{MEM}[PC+1+Offset]])$

- STI SR, Offset

- $(\mathbf{MEM}[\mathbf{MEM}[PC+1+Offset]] \leftarrow SR)$

Offset = sxt(PCOffset9)

# Project1 Specifics


---

- Subset of instructions
    - ALU (ADD, NOT, AND) ; LEA
    - All instructions take 5 clock cycles
  - Block level inputs and outputs
    - Some inputs and outputs invalid: Will become clear in next project(s)
  - LC3 is unpipelined
    - Each instruction goes through the 5 cycles  
Fetch → Decode → Execute → Writeback → UpdatePC
    - No typical pipeline issues like control and data dependence .. FOR NOW !!
-
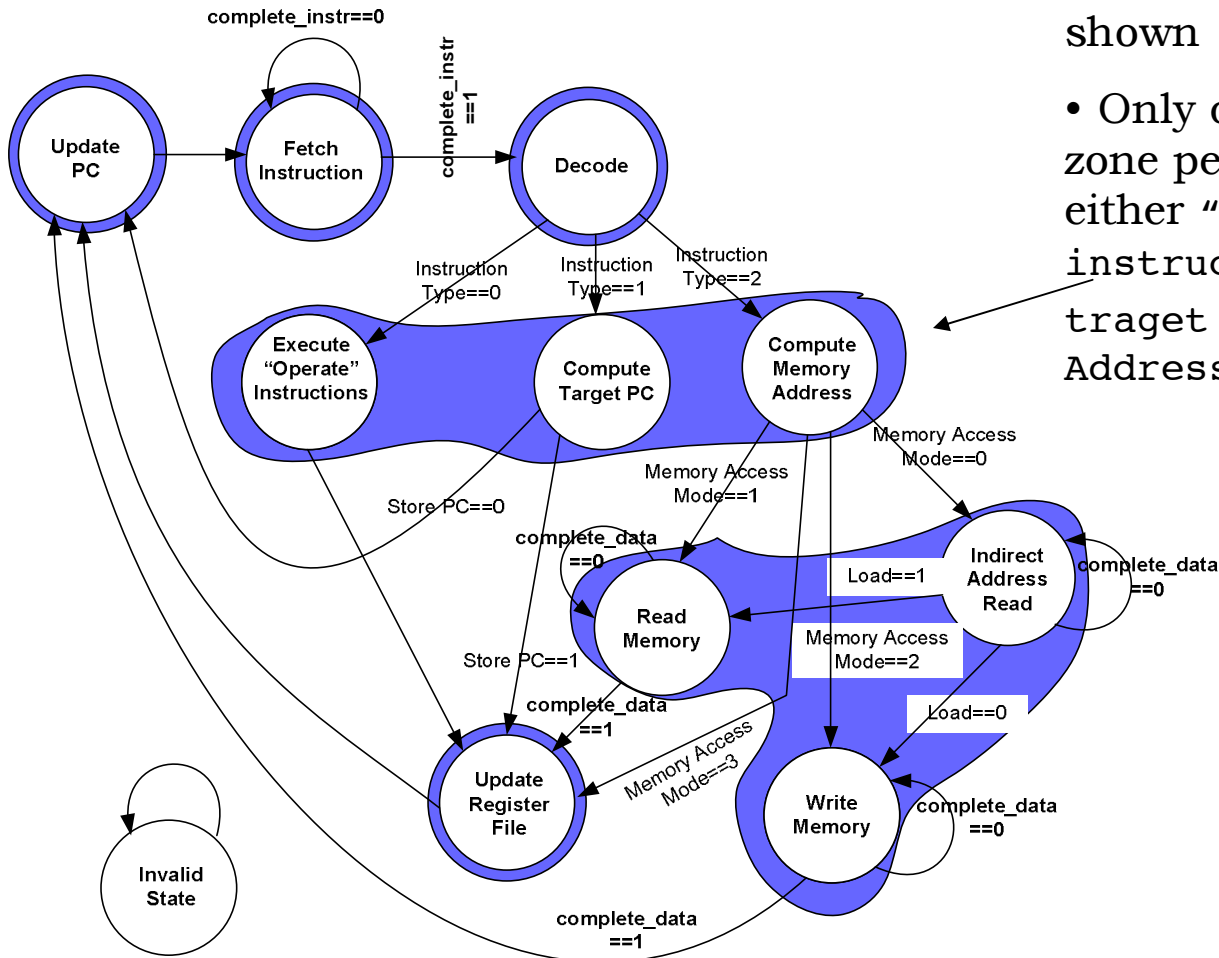
# LC-3 Components (Base States)

- 5 base pipeline “zones” + memory shown

- Only one of the operations in a zone performed in a clock cycle eg. either “execute operate instruction” OR “compute target PC” OR “Compute Memory Address”



# ADD/NOT/AND Base States

Example:

IR = 5220 (AND R1, R0, #0)

DR = 1, SR1 = 0, Imm = 0

1. Fetch Unit loads instruction from memory

IR = IMem[PC] = 5220

2. Decode Unit determines the operands using IR  
E\_control, W\_Control created

3. Execute Unit applies operands to ALU using E\_Control


aluout = R0 & 0

4. Result stored in Register File

R1 = aluout

5. PC incremented

PC = PC + 1

 

**Example:**  
 IR = EC08 (LEA R6,#8)  
 DR = 6, Imm = 3

**1.** Fetch Unit loads instruction from memory  
 $IR = IMem[PC] = EC08$


**2.** Decode Unit determines the operands  
 $E\_control, W\_Control$  etc.

**3.** Compute Memory Address with Offset  
 $aluout = PC + 1 + 8$

**4.** Write Memory Address to Reg File  
 $R6 = aluout$

 
**5.** PC incremented  
 $PC = PC + 1$

```
IR = EC08 (LEA R6,#8)
DR = 6, Imm =3
```




1. Fetch Unit loads instruction from memory  
 $IR = IMem[PC] = EC08$
2. Decode Unit determines the operands  
 $E\_control, W\_Control$  etc.
3. Compute Memory Address with Offset  
 $aluout = PC + 1 + 8$
4. Write Memory Address to Reg File  
 $R6 = aluout$
5. PC incremented  
 $PC = PC + 1$

# LC3 Internals FETCH

 


- On reset: `pc = 3000`; `npc = 3001`;
- Signals of Importance
  - `enable_fetch` and `enable_updatePC`
  - `PC` = Program Counter of instruction being fetched
  - `npc = PC + 1`
  - `Imem_rd` = enable for Instruction Mem Read
- Ignore
  - `br_taken` = if 1 `PC = taddr` else `PC = PC+1`
  - `taddr` = new PC if branch is taken
- if `enable_fetch=1` `Imem_rd=1` asynchronously else `Imem_rd=Z` (HIGH IMPEDANCE)
- `PC`, `npc`, `Imem_rd` updated only when `enable_updatePC=1`

# LC3 Internals FETCH

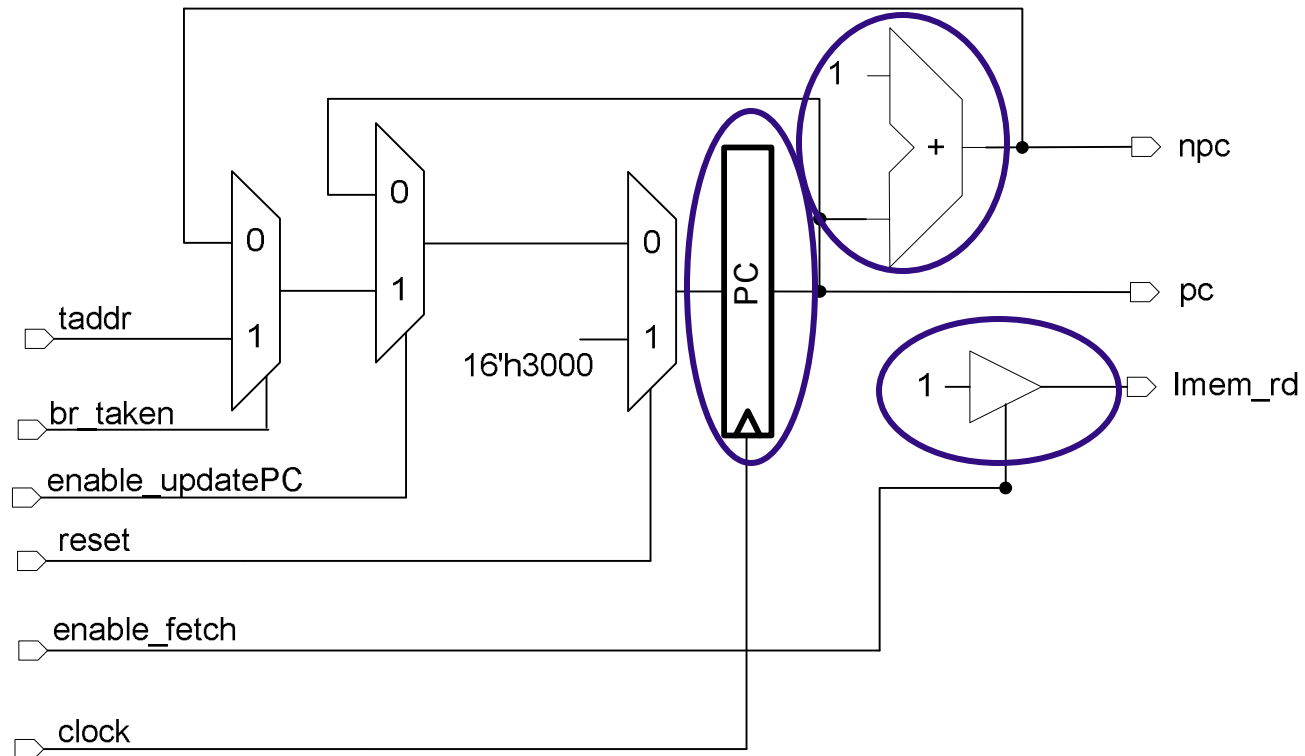

# LC3 Internals DECODE

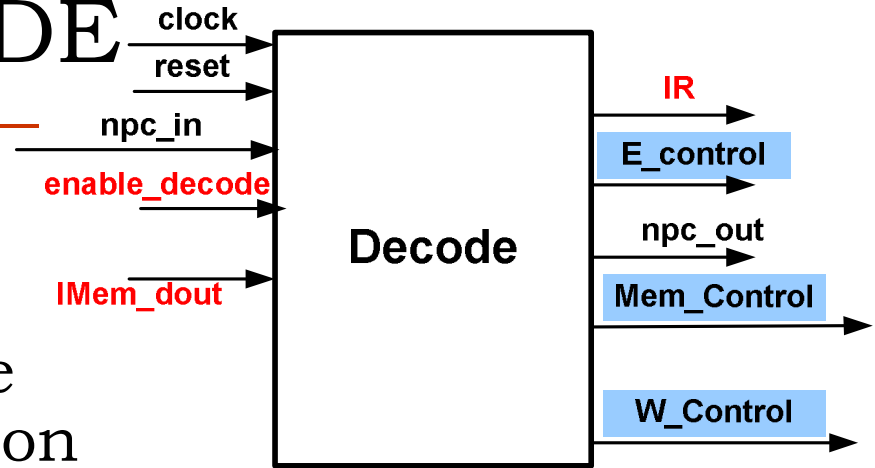

- Creates relevant control signals using IMem\_dout
- Controls uniquely configure datapath for given instruction
- Signals of Importance
  - enable\_decode: master enable
  - E\_Control = Execute Block Control
  - W\_Control = Writeback Block Control
  - IR = Instruction Register: Reflects contents of Imem\_dout
  - npc\_out: reflects contents of npc\_in
- Ignore
  - Mem\_Control = Control signals for memory related operations
- All outputs created synchronously when enable\_decode=1
- On reset, all outputs go to 0



# LC3 Internals DECODE

---

- W\_Control
  - 2 bits
  - Control for Writeback
  - Function of IR[15:12]
  - Enables choice between aluout, memout, pcout for writes to register file
  - We shall focus only on ALU and LEA instructions  
W\_control either 0 (ALU) or 2 (LEA)

Operation	mode	W Control
ADD	0	0(aluout)
	1	0(aluout)
AND	0	0(aluout)
	1	0(aluout)
NOT		0(aluout)
BR		0
JMP		0
LD		1(memout)
LDR		1(memout)
LDI		1(memout)
LEA		2(pcout)
ST		0
STR		0
STI		0

# LC3 Internals DECODE

---


- E\_Control:{alu\_control, pcselect1, pcselect2, op2select}

IR[15:12]	IR[5]	E_Control			
		alu_control [2]	pcselect1 [2]	pcselect2 [1]	op2select [1]
ADD	0	<b>0</b>	-	-	VSR2 ( <b>1</b> )
	1	<b>0</b>	-	-	imm5 ( <b>0</b> )
AND	0	<b>1</b>	-	-	VSR2 ( <b>1</b> )
	1	<b>1</b>	-	-	imm5 ( <b>0</b> )
NOT		<b>2</b>	-	-	-
BR		-	offset9 ( <b>1</b> )	npc ( <b>1</b> )	-
JMP		-	0 ( <b>3</b> )	VSR1 ( <b>0</b> )	-
LD		-	offset9 ( <b>1</b> )	npc ( <b>1</b> )	-
LDR		-	offset6 ( <b>2</b> )	VSR1 ( <b>0</b> )	-
LDI		-	offset9 ( <b>1</b> )	npc ( <b>1</b> )	-
LEA		-	offset9 ( <b>1</b> )	npc ( <b>1</b> )	-
ST		-	offset9 ( <b>1</b> )	npc ( <b>1</b> )	-
STR		-	offset6 ( <b>2</b> )	VSR1 ( <b>0</b> )	-
STI		-	offset9 ( <b>1</b> )	npc ( <b>1</b> )	-

---


# LC3 Internals DECODE

---

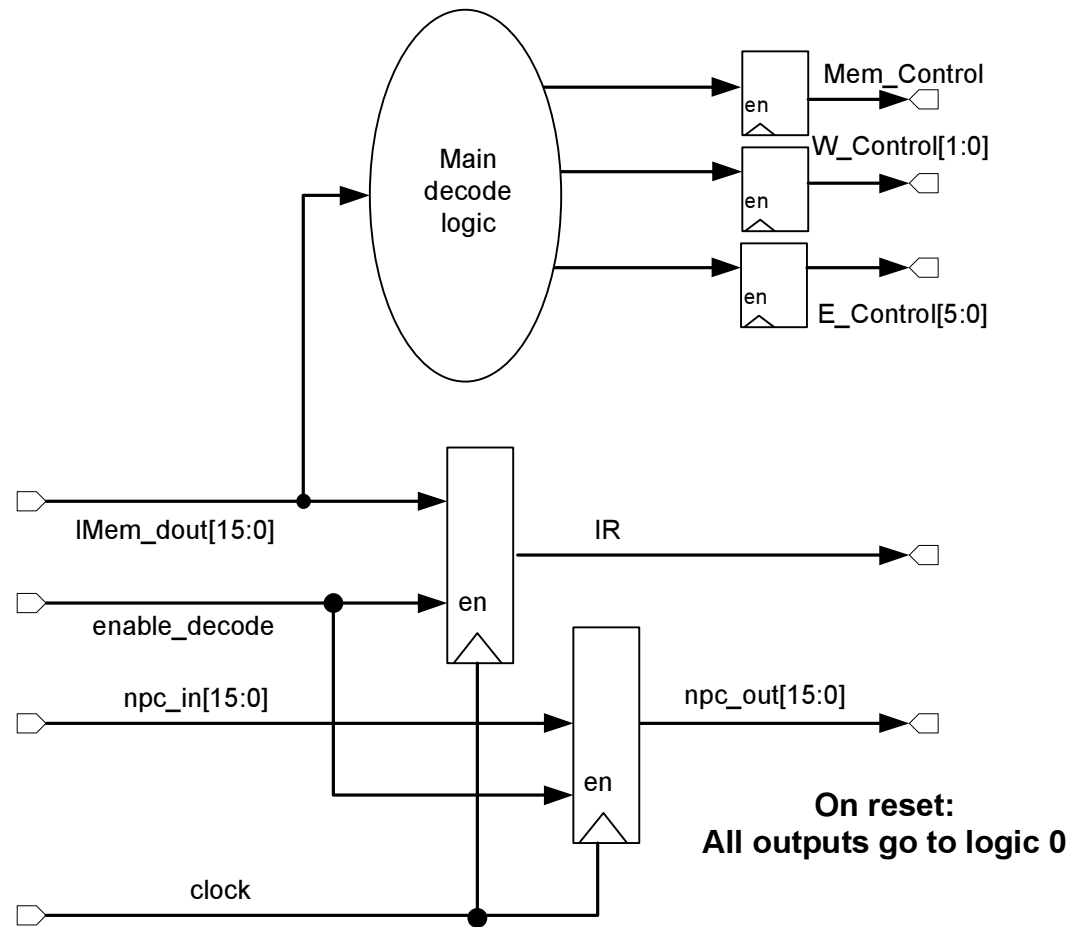
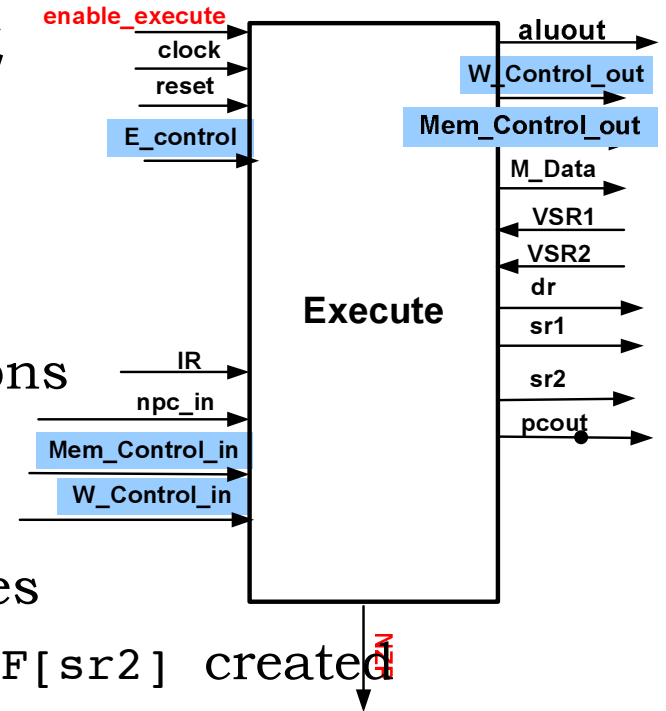
# LC3 Internals EXECUTE

- Closely coupled with the Writeback Block which provides all the relevant data values for register related operations
- Signals of importance
  - `sr1` & `sr2` = source register addresses
  - `VSR1` & `VSR2` = values of `RF[sr1]` & `RF[sr2]` created asynchronously in Writeback
  - `aluout` = result of alu operation (ADD, NOT, AND)
  - `pcout` = result of pc related operation (BR, JMP, LEA)
  - `dr` = destination register address
  - `W_control_out`: reflects synchronously `W_control_in`
- Ignore
  - `M_Data` = RF value to be written to memory
  - `Mem_control_in`, `NZP`, `Mem_control_out`



# LC3 Internals EXECUTE

---

( [DR] ← [SR1] **aluop** [SR2] )


( [DR] ← [SR1] **aluop sxt**(Imm) )

**LEA** ( [DR] ← PC+1+sxt(PCOffset9) )


**DR:** IR[11:9] (**synchronous**)

**SR1:** IR[8:6] (**asynchronous**)

**SR2:** IR[2:0] (**asynchronous**)

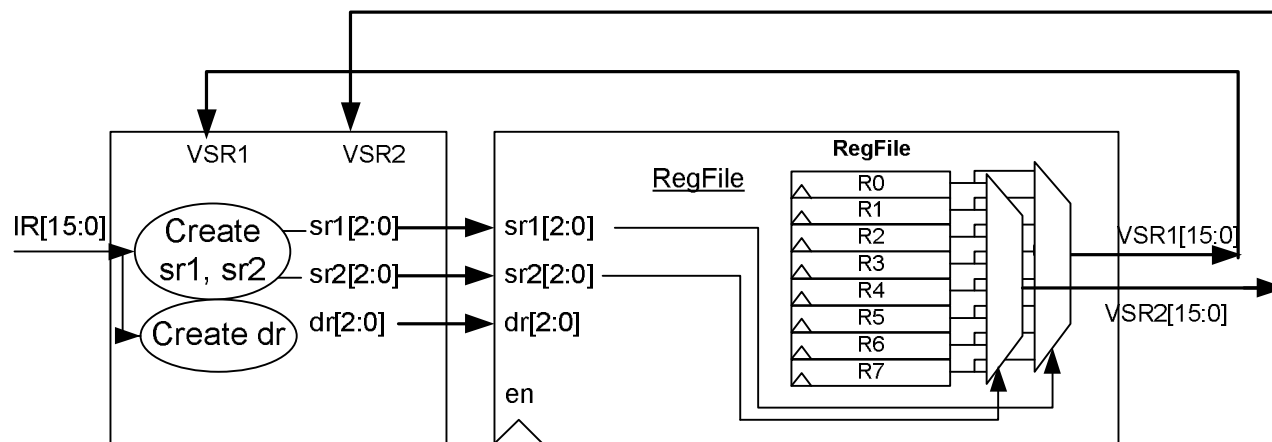

# LC3 Internals EXECUTE

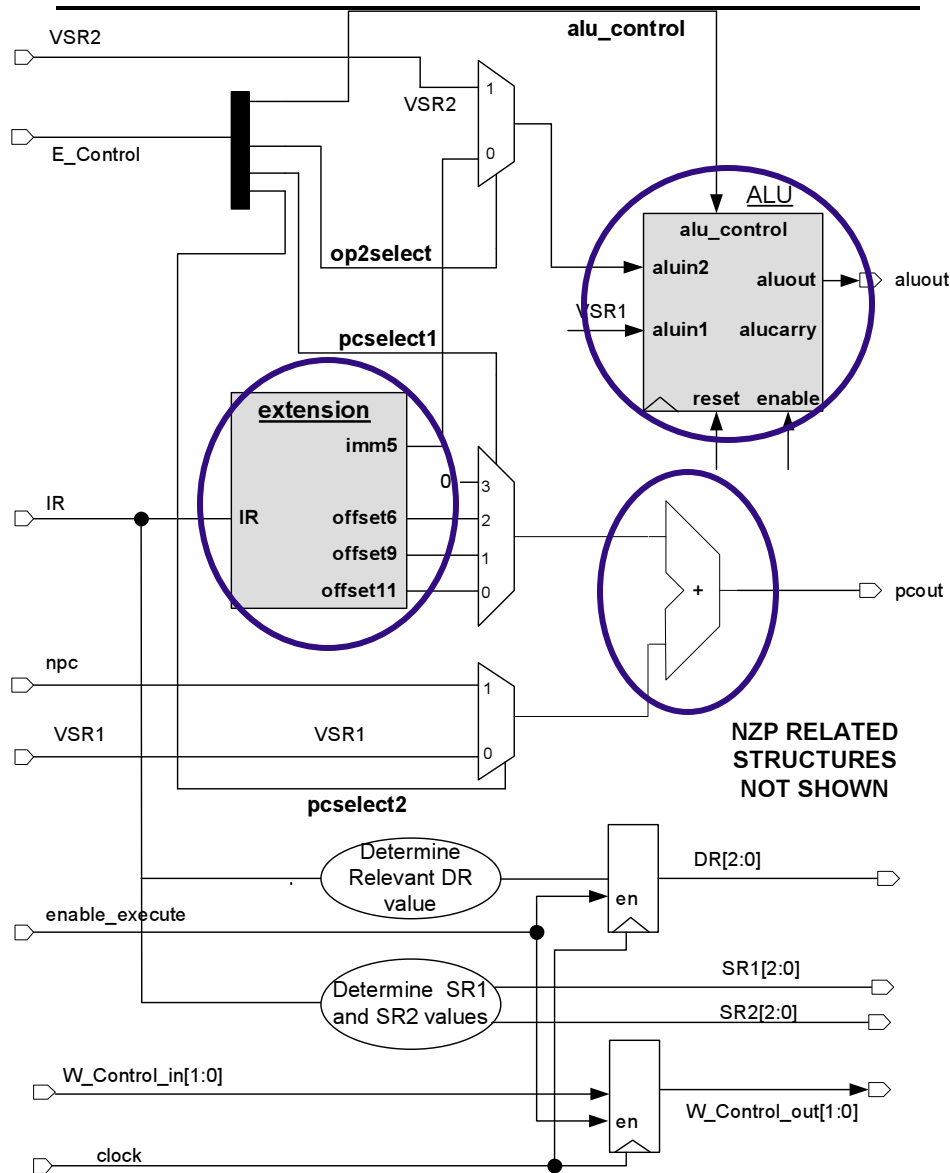

**imm5** = {11{IR[4], IR[4:0]}}

**offset6** = {10{IR[5], IR[5:0]}}

**offset9** = {7{IR[8], IR[8:0]}}

**offset11** = {5{IR[10], IR[10:0]}}



**On reset,**

**aluout, pcout, W\_control\_out, dr**  
**go to 0**



# ALU Operation Instructions

---


ADD

  

AND

  

NOT

 

# Memory Operations


---

	15	12	11	9	8	6	5	4	3	2	0
LD	0	0	1	0	DR	PCOffset9					
LDR	0	1	1	0	DR	BaseR		Offset6			
LDI	1	0	1	0	DR	PCOffset9					
LEA	1	1	1	0	DR	PCOffset9					
ST	0	0	1	1	SR	PCOffset9					
STR	0	1	1	1	SR	BaseR		Offset6			
STI	1	0	1	1	SR	PCOffset9					




# LC3 Internals WRITEBACK

---

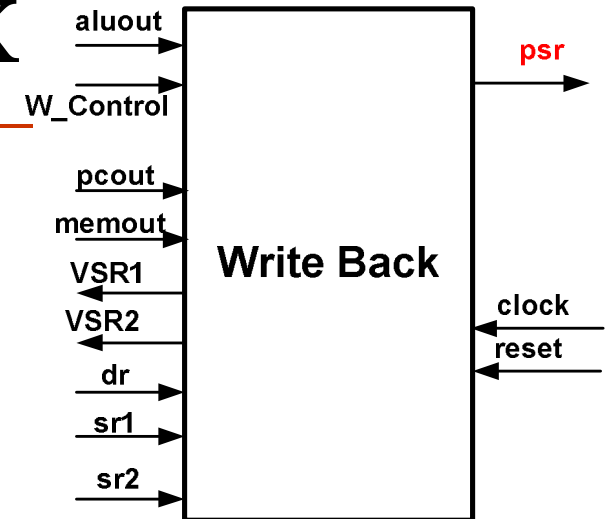


- Contains register file (RF/RegFile)
    - Addressed using `sr1`, `sr2` and `dr`
    - Writes either `aluout`, `pcout` OR `memout` based on `W_control_in` value
    - Synchronous Writes to RF with `dr`  
`RegFile[dr] = DR_in`
    - Asynchronous Reads from RF using `sr1`&`sr2`
  - Important Signals:
    - `enable_writeback`: master enable
    - `aluout`, `pcout`, `memout`:
    - `W_Control`
    - `sr1`, `sr2`, `dr`, `VSR1`, `VSR2`
  - Ignore:
    - PSR: Program Status Register
-

# LC3 Internals WRITEBACK

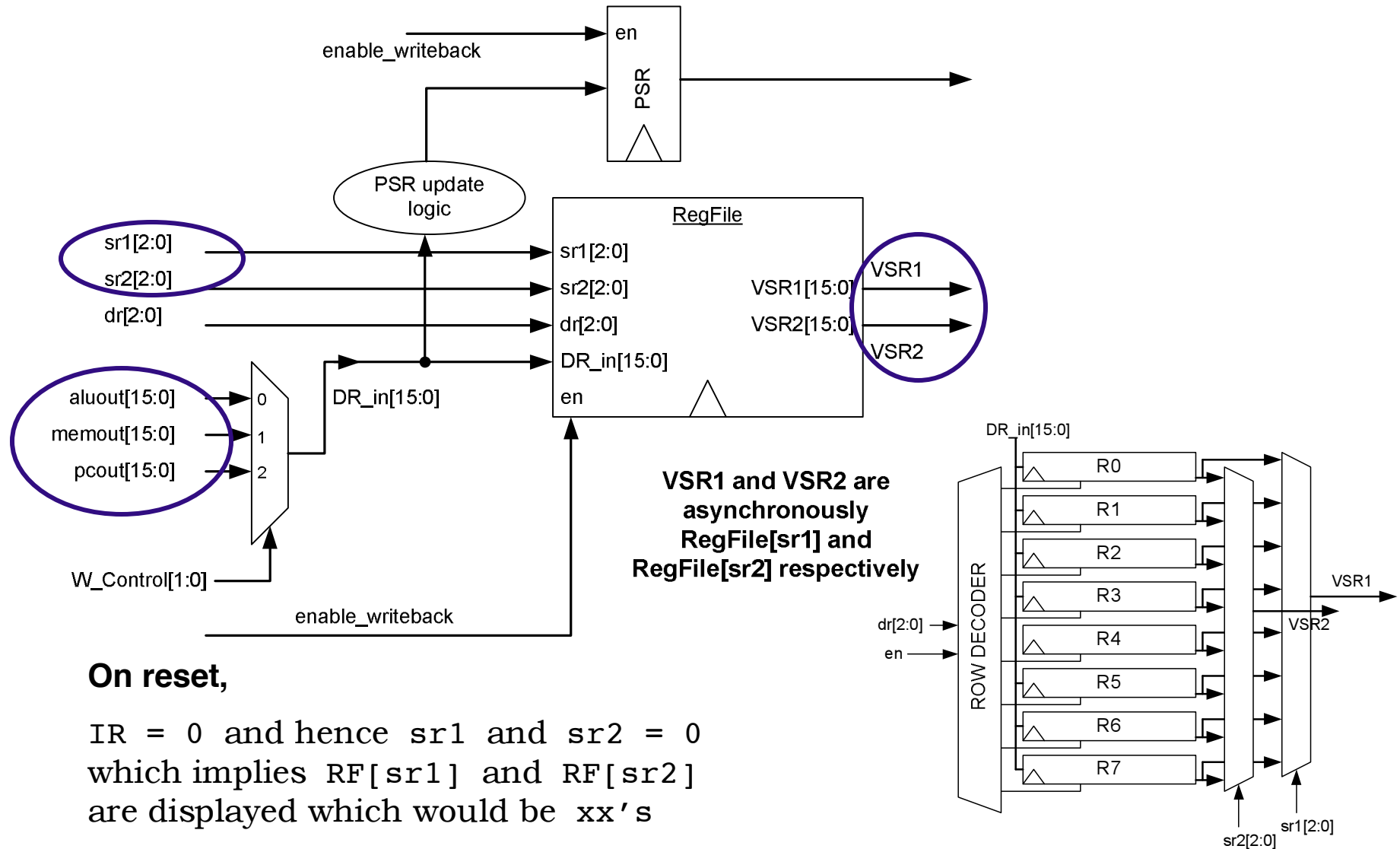

# LC3 Internals CONTROL

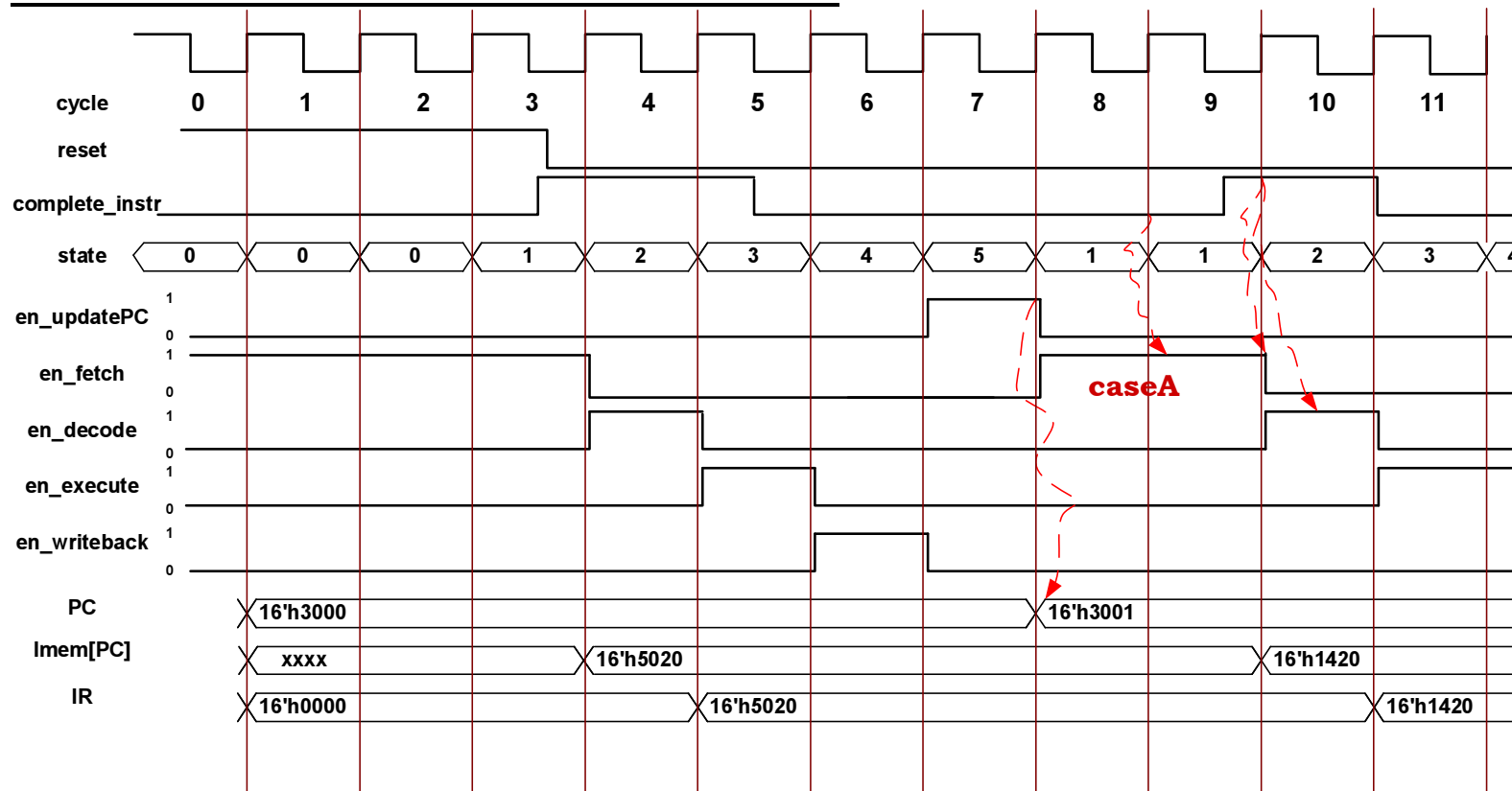

**@3000: 5020 (AND R0 R0 #0); @3001: 1420 (ADD R2 R0 #0)**

- Sensitivity to complete\_instr signal only:  
transition from state: 1→2 only when complete\_instr == 1 at posedge of clock
- PC = Program Counter ; IR = Instruction Register ; IMem = Instruction Memory ;

# Detailed Timing Example

---

<b>@3000: 5020 (AND R0 R0 #0);</b>	<b>@3001: 1422 (ADD R2 R0 #2)</b>
<b>@3002: 1820 (ADD R1 R2 R0);</b>	<b>@3003: EC03 (LEA R6 #-2)</b>

**FETCH** (after reset has gone to 0)

**in:** enable\_fetch = 1 ; pc = 3000 ; npc = 3001 ;  
**out:** IMem\_rd = 1 ;

## DECODER

**in:** IMem\_dout = IMem[3000] = 5020 ; npc\_in = 3001 ;  
enable\_decoder = 1 ;  
**out:** npc\_out = 3001; IR = 5020 ; W\_Control = 0 (aluout) ;  
alu\_control = 1; pcselect1 = 0; pcselect2 = 0; op2select = 0 (imm5)  
=> E\_Control = [6'b01\_0000]

## EXECUTE

**in:** E\_Control = [6'b01\_0000]; W\_Control\_in = 0 ; npc\_in = 3001 ;  
IR = 5020 ; enable\_execute = 1 ;  
VSR1 = R0 = xxx ; VSR2 = R0 = xxx ;  
**out:** sr1 = 0; sr2 = 0 ;  
dr = 0 ; W\_Control\_out = 0 ; aluout = VSR1 & sxt(Imm5) = R0&0 = 0

## WRITEBACK

**in:** dr = 0 ; W\_Control = 0 ; aluout = 0 ; enable\_writeback = 1 ;  
**out:** RegFile[dr] = aluout = 0 => R0 = 0

## UPDATEPC

**in:** enable\_updatePC = 1 ; **out:** pc = 3001 ; npc = 3002

---

# Detailed Timing Example

---

**@3000: 5020 (AND R0 R0 #0);**    **@3001: 1422 (ADD R2 R0 #2)**  
**@3002: 1820 (ADD R1 R2 R0);**    **@3003: EC03 (LEA R6 #-2)**

## **FETCH**

**in:** enable\_fetch = 1 ; pc = 3001 ; npc = 3002 ;  
**out:** IMem\_rd = 1 ;

## **DECODER**

**in:** IMem\_dout = IMem[3001] = 1420 ; npc\_in = 3002 ;  
enable\_decoder = 1 ;  
**out:** npc\_out = 3002; IR = 1420 ; W\_Control = 0 (aluout) ;  
alu\_control = 0; pcselect1 = 0; pcselect2 = 0; op2select = 0 (imm5)  
=> E\_Control = [6'b01\_0000]

## **EXECUTE**

**in:** E\_Control = [6'b01\_0000]; W\_Control\_in = 0 ; npc\_in = 3002 ;  
IR = 1420 ; enable\_execute = 1 ;  
VSR1 = R0 = 0 ; VSR2 = R0 = 0 ;  
**out:** sr1 = 0; sr2 = 0 ;  
dr = 0 ; W\_Control\_out = 0 ; aluout = VSR1 + sxt(Imm5) = 0 + 2 = 2

## **WRITEBACK**

**in:** dr = 2 ; W\_Control = 0 ; aluout = 0 ; enable\_writeback = 1 ;  
**out:** RegFile[dr] = aluout = 2 => R2 = 2

## **UPDATEPC**

**in:** enable\_updatePC = 1 ; **out:** pc = 3002 ; npc = 3003

---

# Detailed Timing Example

---

**@3000: 5020 (AND R0 R0 #0);    @3001: 1422 (ADD R2 R0 #2)**  
**@3002: 1820 (ADD R1 R2 R0);    @3003: EC03 (LEA R6 #-2)**

## **FETCH**

**in:** enable\_fetch = 1 ; pc = 3002 ; npc = 3003 ;  
**out:** IMem\_rd = 1 ;

## **DECODER**

**in:** IMem\_dout = IMem[3001] = 1820 ; npc\_in = 3003 ;  
enable\_decoder = 1 ;  
**out:** npc\_out = 3003; IR = 1820 ; W\_Control = 0 (aluout) ;  
alu\_control = 0; pcselect1 = 0; pcselect2 = 0; op2select = 1 (VSR2)  
=> E\_Control = [6'b01\_0001]

## **EXECUTE**

**in:** E\_Control = [6'b01\_0001]; W\_Control\_in = 0 ; npc\_in = 3003 ;  
IR = 1820 ; enable\_execute = 1 ;  
VSR1 = R2 = 2 ; VSR2 = R0 = 0 ;  
**out:** sr1 = 0; sr2 = 0 ;  
dr = 0 ; W\_Control\_out = 0 ; aluout = VSR1 + VSR2 = 2 + 0 = 2

## **WRITEBACK**

**in:** dr = 1 ; W\_Control = 0 ; aluout = 0 ; enable\_writeback = 1 ;  
**out:** RegFile[dr] = aluout = 0 => R1 = 2

## **UPDATEPC**

**in:** enable\_updatePC = 1 ; **out:** pc = 3003 ; npc = 3004

---

# Detailed Timing Example

---

@3000: 5020 (**AND** R0 R0 #0);    @3001: 1422 (**ADD** R2 R0 #2)  
@3002: 1820 (**ADD** R1 R2 R0);    @3003: **EDFE** (**LEA** R6 #-2)

## FETCH

in: enable\_fetch = 1 ; pc = 3003 ; npc = 3004 ;  
out: IMem\_rd = 1 ;

## DECODE

in: IMem\_dout = IMem[3001] = **EDFE**; npc\_in = 3004 ;  
    enable\_decoder = 1 ;  
out: npc\_out = 3004 ; IR = **EDFE**; W\_Control = 2 (pcout) ;  
    alu\_control=0; pcselect1 = 1(**offset9**); pcselect2 = 1(**npc**); op2select = 0  
    => E\_Control = [6'b01\_0110]

## EXECUTE

in: E\_Control = [6'b01\_0110]; W\_Control\_in = 2 ; npc\_in = 3004 ;  
    IR = **EDFE**; enable\_execute = 1 ;  
    VSR1 = R0 = 0 ; VSR2 = R0 = 0 ;  
out: sr1 = 0; sr2 = 0 ;  
    dr = 6 ; W\_Control\_out=2 ; aluout = npc + **sxt(offset9)** = 3004 + -2 = 3002


## WRITEBACK

in: dr = 6 ; W\_Control = 0 ; aluout = 0 ; enable\_writeback = 1 ;  
out: RegFile[dr] = aluout = 0 => R6 = 3002

## UPDATEPC

in: enable\_updatePC = 1 ; out: pc = 3002 ; npc = 3003

---

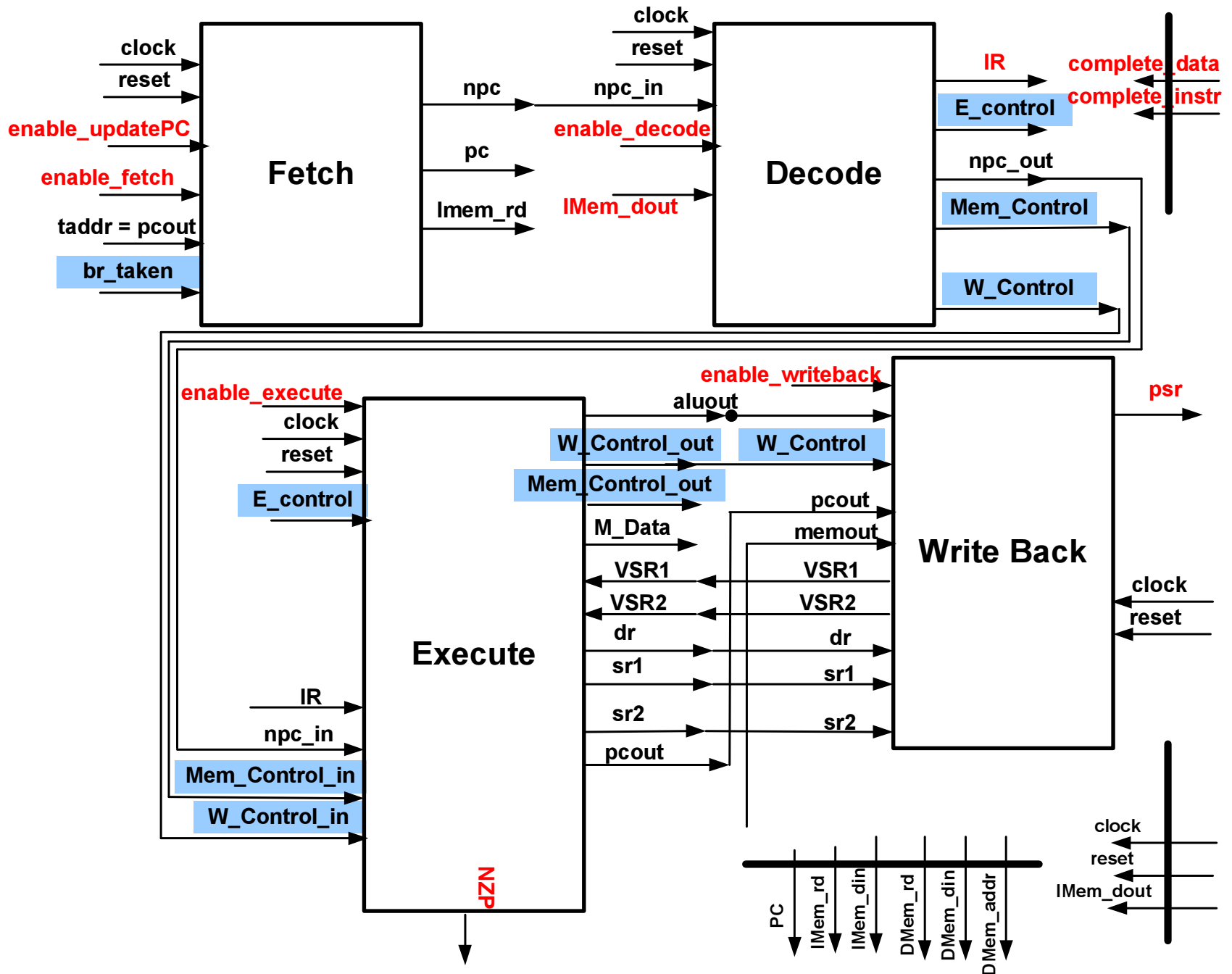



# Testing Considerations

---

- Where Do you start?
    - Inputs and Outputs to the design & their constraints
    - Timing of instructions (5 cycles)
    - Understand controller timing
  - Basic Checks
    - Reset Behavior (Each block has a particular behavior)
    - Completion of instructions and time taken
    - Operational Correctness i.e. results are right
    - Register File correctness
  - Further issues
    - Smart use of data values: use inputs that give you maximum information
    - Sequence of instructions: ADD→NOT→AND→ADD with dr in one instruction being the sr1/2 in the next.
-